

005/2016

Maximum : 100 marks

Time : 1 hour and 15 minutes

- Kirchhoff's Voltage Law (KVL) is a restatement of :
(A) Principle of conservation of charge (B) Principle of conservation of energy
(C) Both (A) and (B) (D) None of the above
- If the number of turns of a coil is doubled, its inductance :
(A) Decreases two times (B) Decreases four times
(C) Increases two times (D) Increases four times
- Two batteries having emf's of 10 V and 7 V and internal resistances 2Ω and 3Ω respectively are connected in parallel across a load of resistance of 1Ω . The current drawn by the load is :
(A) 3 A (B) 1 A
(C) 4 A (D) 2 A
- A square coil of 10 cm side and with 100 turns is rotated at a uniform speed of 1000 revolutions per minute about an axis at right angles to a uniform magnetic field having a flux density of 0.5 wb/m^2 . The instantaneous value of induced emf when the plane of the coil is parallel to the plane of the field is :
(A) Zero (B) 25.3 V
(C) 52.3 V (D) 40.5 V
- In an RLC series circuit, $R=2\Omega$, $X_L=4\Omega$ and $X_C=6\Omega$. The current is 5 A. The applied voltage in the circuit is :
(A) 14.14 V (B) 10.44 V
(C) 141.4 V (D) 1.414 V
- A current of 10 A flows in a circuit with 30° angle of lag when the applied voltage is 100 V. The resistance, reactance and impedance are :
(A) 8.666Ω , 5Ω , 10Ω (B) 10Ω , 5Ω , 0.866Ω
(C) 10Ω , 0.866Ω , 5Ω (D) 0.866Ω , 10Ω , 5Ω
- A wire is placed parallel to the lines of force in a magnetic field and a current flows in this wire. Then :
(A) The wire experiences a force in the direction of the magnetic field
(B) The wire does not experience any force
(C) The wire experiences a force in a direction opposite to the magnetic field
(D) The wire experiences a force in a direction perpendicular to the magnetic field

8. If a 10Ω resistance is connected to an a.c. supply $v = 100 \sin(314t + 37^\circ)$ V, the power dissipated by the resistance is :
- (A) 10,000 W (B) 1000 W
(C) 250 W (D) 500 W
9. A three phase, four wire 100 V (L-L) system supplies a balanced star connected load having impedance of $10 \angle -30^\circ \Omega$ in each phase. How much current is flowing through the neutral?
- (A) 10 A (B) 1 A
(C) 0 A (D) 5.77 A
10. If T_a is the torque and I_a , the armature current for a DC series motor, which of the following relation is valid, after core saturation?
- (A) $T_a \propto I_a^2$ (B) $T_a \propto \frac{1}{(I_a)^2}$
(C) $T_a \propto \frac{1}{I_a}$ (D) $T_a \propto I_a$
11. The permissible flux density of cold rolled grain oriented steel used for transformer core is around :
- (A) 1.7 wb/m² (B) 2.7 wb/m²
(C) 3.5 wb/m² (D) 0.5 wb/m²
12. The nameplate of an energy meter reads '1 KWh = 15,000 revolutions'. If the meter completes 150 revolutions during 50 seconds, what is the power in the circuit?
- (A) 100 W (B) 720 W
(C) 600 W (D) 1000 W
13. An ammeter with full scale deflection current of $100 \mu\text{A}$ (micro ampere) and internal resistance of 100Ω is required to measure a maximum current of 10 mA. The shunt resistance value is :
- (A) 1.10 Ω (B) 1.01 Ω
(C) 1.11 Ω (D) 1.00 Ω
14. If the moving coil of a voltmeter consists of 100 turns around on a square former which has a length of 30 mm and flux density in the air gap is 0.09 wb/m^2 . The deflecting torque on the coil when carrying a current of 10 mA is :
- (A) $27 \times 10^{-6} \text{ Nm}$ (B) $8.1 \times 10^{-6} \text{ Nm}$
(C) $2.7 \times 10^{-6} \text{ Nm}$ (D) $81 \times 10^{-6} \text{ Nm}$
15. A 5 A, 230 V meter on full load, unity power factor test makes 72 revolutions in 360 seconds. If the normal disc speed is 600 rev/KWh, what is the percentage error?
- (A) 0.12% (B) 1.2%
(C) 0.434% (D) 4.17%

16. In a moving iron instrument, the deflection torque, T_d is :
- Directly proportional to square of current
 - Inversely proportional to square of current
 - Directly proportional to current
 - Inversely proportional to current
17. Inductance affects the direct current (d.c.) flow :
- only at the time of turning off
 - only at the time of turning on
 - at the time of turning on and off
 - at all the time of operation
18. For a sine wave with peak value E_{max} , the average value is :
- $0.636 E_{max}$
 - $0.707 E_{max}$
 - $0.434 E_{max}$
 - $1.414 E_{max}$
19. The ratio of starting torque to full load torque is least in :
- DC series motor
 - DC shunt motor
 - DC compound motor
 - None of the above
20. The iron core from an iron-cored coil is removed so that it becomes air-cored. The inductance of the coil :
- remains the same
 - becomes zero
 - decreases
 - increases
21. The forbidden energy band gap for Germanium is :
- 0.12 eV
 - 0.32 eV
 - 0.72 eV
 - 7.2 eV
22. When the reverse bias is applied to a junction diode :
- The minority carrier current is increased
 - The majority carrier current is increased
 - The potential barrier is lowered
 - The potential barrier is increased
23. In a full-wave rectifier which uses two ideal diodes, the approximate relationship are :
- $V_{dc} = \frac{V_m}{\pi}$, $PIV = 2V_m$
 - $V_{dc} = \frac{2V_m}{\pi}$, $PIV = 2V_m$
 - $V_{dc} = \frac{2V_m}{\pi}$, $PIV = V_m$
 - $V_{dc} = \frac{V_m}{\pi}$, $PIV = V_m$
24. A forward biased silicon diode when carrying a negligible current has a voltage drop of 0.65 V. When the current through the diode is increased to 1A, it dissipates 500 mW. The ON-resistance of the diode is :
- 0.325 Ω
 - 0.5 Ω
 - 0.65 Ω
 - 0.77 Ω

25. Which of the following statement is correct for the basic transistor configurations?
- (A) CB configuration has low input impedance and a low current gain
 - (B) CC configuration has low output impedance and a high voltage gain
 - (C) CE configuration has very poor voltage gain but very high input impedance
 - (D) The current gain of CB configuration is higher than the current gain of CC configuration
26. A Bipolar Junction transistor is said to be operating in saturation region if
- (A) Emitter junction is forward biased and collector junction is reverse biased
 - (B) Emitter junction is reverse biased and collector junction is forward biased
 - (C) Both the junctions are forward biased
 - (D) Both the junctions are reverse biased
27. Pinch - off voltage of a JFET is :
- (A) The gate-to-source voltage at which the drain current starts to saturate
 - (B) The drain-to-source voltage at which the drain current becomes zero
 - (C) The channel-to-gate voltage at which the drain current becomes zero
 - (D) The channel-to-gate reverse bias voltage at which the drain current starts to saturate
28. The best material for the gate region construction of a MOSFET is :
- (A) High purity silicon
 - (B) High purity silica
 - (C) Epitaxial grown silicon
 - (D) Heavily doped polycrystalline silicon
29. The common-emitter short circuit current gain β of a BJT :
- (A) Is a monotonically increasing function of I_c
 - (B) Is a monotonically decreasing function of I_c
 - (C) Increases with I_c for low values of I_c , reaches a maximum and then decreases with further increase in I_c
 - (D) Is not a function of I_c
30. For full-wave rectification, a four-diode bridge rectifier is claimed to have the following advantages over a two-diode circuit :
- (1) Less expensive transformer
 - (2) Smaller size transformer and
 - (3) Suitability for higher voltage application
- Of these
- (A) Only (1) and (2) are true
 - (B) Only (1) and (3) are true
 - (C) Only (2) and (3) are true
 - (D) (1), (2) and (3) are true
31. A 1 MHz sinusoidal carrier wave is amplitude modulated by a sine wave of period 100 μ s. Which of the following frequencies will not be present in the modulated output signal?
- (A) 990 KHz
 - (B) 1000 KHz
 - (C) 1010 KHz
 - (D) 1020 KHz

32. Two non-inverting amplifiers, one having a unity gain and the other having a gain of 10, are made using identical operational amplifiers. As compared to the unity gain amplifier, the amplifier circuit with gain 10 has :
- (A) Less negative feedback
(B) Greater input impedance
(C) More bandwidth
(D) None of these
33. The image frequency of the AM super heterodyne receiver when it is tuned to receive a radio station operating at 628 KHz is :
- (A) 1538 KHz
(B) 1256 KHz
(C) 1083 KHz
(D) 855.5 KHz
34. A 741 type op-amp has a gain bandwidth product of 1 MHz. A non-inverting amplifier using this op-amp and having a voltage gain of 20 dB will exhibit a -3dB bandwidth of :
- (A) 50 KHz
(B) 100 KHz
(C) $\frac{1000}{17}$ KHz
(D) $\frac{1000}{70.7}$ KHz
35. How many number of NOR gates are required to realise an AND function?
- (A) 2
(B) 3
(C) 4
(D) 5
36. Simplified form of the logic expression :
 $(X + Y + Z)(X + \bar{Y} + Z)(X + \bar{Y} + \bar{Z})$
- (A) X
(B) $XY + \bar{Z}$
(C) $X + \bar{Y}Z$
(D) $\bar{X}Y + \bar{Z}$
37. The C - band is :
- (A) 1 to 2 GHz
(B) 2 to 4 GHz
(C) 4 to 8 GHz
(D) 8 to 12 GHz
38. If D is the distance between two co-channel cells and R is the cell radius, then $\frac{D}{R}$ is known as :
- (A) Co-channel interference reduction factor
(B) Adjacent channel interference reduction factor
(C) Adjacent and co-channel interference reduction factor
(D) None of these
39. The cell using different carrier frequencies in a cluster is :
- (A) Co-channel cell
(B) Adjacent cell
(C) Micro cell
(D) Macro cell
40. Which of the following is the correct statement in connection with satellite communication?
- (A) A satellite is stationary in the outer - space
(B) Co-located earth stations are used for frequency diversity
(C) Satellites are allocated so that it is impossible for two earth stations not to face the same satellite
(D) A satellite earth station must have as many receiver chains as there are carriers transmitted to it

41. Two forces of equal magnitude ' P ' act at an angle ' θ ' to each other. Their resultant will be :
- (A) $2P \sin \frac{\theta}{2}$ (B) $2P \cos \frac{\theta}{2}$
 (C) $P \cos \frac{\theta}{2}$ (D) $P \sin \frac{\theta}{2}$
42. The unit of energy in SI system of units is :
- (A) watt (B) dyne
 (C) joule (D) kg-m
43. The moment of inertia of a thin disc of mass ' m ' and radius ' r ', about an axis passing through its centre of gravity and perpendicular to the plane of the disc is :
- (A) $0.5 mr^2$ (B) mr^2
 (C) $0.25 mr^2$ (D) $2 mr^2$
44. The ratio of limiting friction to the normal reaction between the two bodies is defined as :
- (A) Sliding friction (B) Angle of friction
 (C) Friction of resistance (D) Coefficient of friction
45. The loss of kinetic energy during the impact of collision of two inelastic bodies (mass = m_1, m_2 , velocities = u_1, u_2) is given by :
- (A) $\frac{m_1 m_2}{(m_1 + m_2)} (u_1 - u_2)^2$ (B) $\frac{m_1 m_2}{2(m_1 + m_2)} (u_1 - u_2)^2$
 (C) $\frac{m_1 m_2}{2(m_1 + m_2)} (u_1 - u_2)$ (D) $\frac{m_1 m_2}{2(m_1 - m_2)} (u_1 - u_2)^2$
46. The maximum deflection at the centre of a simply supported beam of length ' l ' with a uniformly distributed load w /unit length is given by :
- (A) $\frac{5wl^3}{192 EI}$ (B) $\frac{5wl^3}{384 EI}$
 (C) $\frac{5wl^4}{384 EI}$ (D) $\frac{5wl^4}{192 EI}$
47. If the momentum of a given body is doubled, its kinetic energy will :
- (A) Increase by four times (B) Increase by two times
 (C) Increase by eight times (D) Gets halved
48. For a given velocity of projectile, the horizontal range will be maximum when angle of projection with the horizontal is :
- (A) 45° (B) 30°
 (C) 60° (D) 90°