

6/13

050/21

Total Number of Questions : 32

Time : 3.00 Hours

Max. Marks : 200

1. What is meant by forward energy gap in semiconductor and what is the forbidden band gap energy of silicon ? (2 Marks)
2. Define CMRR of an operational amplifier. (2 Marks)
3. Implement NOT gate using NAND gate. (2 Marks)
4. Define modulation index of amplitude modulation. (2 Marks)
5. What is a watchdog timer in a microcontroller ? (2 Marks)
6. What is sampling theorem ? What is the minimum sampling frequency for the proper reconstruction of an analog signal of 1 kHz ? (4 Marks)
7. The collector current of a CE transistor is given as 10 mA and base current is given as 50  $\mu$ A. Define and find  $\beta$  value of the transistor. (4 Marks)
8. What is race-around condition in J-K flip flop ? (4 Marks)
9. Why CAN bus is selected as an industrial bus in embedded systems ? (4 Marks)
10. A system is represented by the equation,  $y(t) = t x(t)$ . Check whether the system is linear or not ? (4 Marks)
11. What is meant by base width modulation ? (5 Marks)
12. Find the transfer function for the given system with output  $y(t)$  and input  $x(t)$  :  
$$\frac{d^2y}{dt^2} + 2\frac{dy}{dt} + y(t) = 5\frac{dx}{dt} + x(t)$$
 (5 Marks)
13. Why optic fiber is preferred over copper cables ? (5 Marks)
14. What is the difference between Harvard architecture and Von Neumann architecture in microprocessors ? (5 Marks)
15. Convert the given decimal number to equivalent binary value :  $127_{10}$  (5 Marks)
16. Draw the inverting amplifier using an op amp. Write the equation for the gain of the amplifier. (5 Marks)
17. Illustrate BPSK signaling scheme for the binary data :  
1 1 0 1 0 1 (5 Marks)
18. Illustrate total internal reflection in optic fiber with Snell's law. (7 Marks)

P.T.O.

050/21

19. Draw and explain the circuit of an astable multivibrator using transistors. (7 Marks)
  20. Explain the concept of a cell in cellular communication. What is frequency reuse? (7 Marks)
  21. What is geostationary satellite? What are conditions for geostationary? Explain with applications. (7 Marks)
  22. Design a Full-Adder using gates. (7 Marks)
  23. Draw and explain superheterodyne receiver system. (10 Marks)
  24. Write a C program to find the factorial of a number. (10 Marks)
  25. Draw and explain a bridge rectifier. Write the expression for ripple factor. (10 Marks)
  26. Explain principle of operation of Switched Mode Power Supply (SMPS) with B/D. (10 Marks)
  27. What is meant by doping? Draw and explain the energy band diagram for n-type and p-type semiconductors. (10 Marks)
  28. Explain the delta modulation with necessary diagrams. (10 Marks)
  29. Design and draw the circuit for a 4-bit ring counter using D flip flop. (10 Marks)
  30. Design a 555 IC based system to generate a waveform with 75% duty cycle. (10 Marks)
  31. Draw and explain a RC coupled CE amplifier. (10 Marks)
  32. Maxwell's equations – state and write equations. (10 Marks)
-